

1. The peak value of an alternating current is 10 A. What is its RMS value?

- A. 5 A
- B. 7.07 A
- C. 10 A
- D. 14.1 A

Answer: B

Explanation:

$$\text{RMS value} = I_0 / \sqrt{2} = 10 / \sqrt{2} \approx 7.07 \text{ A}$$

2. An alternating voltage is given by $V = 220\sqrt{2} \sin(100\pi t)$. What is the RMS value of voltage?

- A. 110 V
- B. 220 V
- C. 440 V
- D. $220\sqrt{2}$ V

Answer: B

Explanation:

$$V_0 = 220\sqrt{2} \rightarrow \text{RMS value} = V_0 / \sqrt{2} = 220 \text{ V}$$

3. In a purely resistive AC circuit, the current and voltage are:

- A. Out of phase by 90°
- B. Out of phase by 180°
- C. In phase
- D. Out of phase by 45°

Answer: C

Explanation:

In a purely resistive circuit, voltage and current are always in phase.

4. In an AC circuit with a capacitor only, the current leads the voltage by:

- A. 0°
- B. 45°
- C. 90°

D. 180°

Answer: C

Explanation:

In a purely capacitive circuit, current leads voltage by 90° .

5. For an inductor of 0.2 H and frequency 50 Hz, the inductive reactance is:

A. 31.4Ω

B. 62.8Ω

C. 15.7Ω

D. 6.28Ω

Answer: A

Explanation:

$$X_L = 2\pi fL = 2 \times \pi \times 50 \times 0.2 = 62.8 \times 0.5 = 31.4 \Omega$$

6. The impedance of an RLC series circuit at resonance is:

A. Infinite

B. Zero

C. Minimum and equal to resistance

D. Maximum and equal to resistance

Answer: C

Explanation:

At resonance, $X_L = X_C \rightarrow$ Impedance $Z = R$ (minimum)

7. In an AC circuit, the power factor is 0.5. The angle between current and voltage is:

A. 0°

B. 30°

C. 60°

D. 90°

Answer: C

Explanation:

$$\text{Power factor} = \cos\phi = 0.5 \rightarrow \phi = \cos^{-1}(0.5) = 60^\circ$$

8. A current $I = 5 \sin(100\pi t)$ flows through a 10Ω resistor. The average power dissipated is:

- A. 62.5 W
- B. 125 W
- C. 250 W
- D. 0 W

Answer: B

Explanation:

$$I_0 = 5 \text{ A} \rightarrow I_{\text{rms}} = 5 / \sqrt{2}$$

$$P = I_{\text{rms}}^2 \times R = (25/2) \times 10 = 125 \text{ W}$$

9. The RMS value of a half-wave rectified sine wave with peak value I_0 is:

- A. I_0
- B. $I_0 / 2$
- C. $I_0 / \sqrt{2}$
- D. $I_0 / 2\sqrt{2}$

Answer: D

Explanation:

$$\text{RMS value of half-wave rectified wave} = I_0 / 2\sqrt{2}$$

10. In an LCR circuit, the quality factor is defined as:

- A. $R / (\omega L)$
- B. $\omega L / R$
- C. $1 / (\omega RC)$
- D. $1 / (\omega^2 LC)$

Answer: B

Explanation:

$$Q = (\omega L) / R \rightarrow \text{Quality factor of an LCR circuit}$$

11. Which of the following is true at resonance in an RLC series circuit?

- A. Voltage across L and C cancel each other
- B. Impedance is maximum
- C. Power factor is zero
- D. Current is minimum

Answer: A

Explanation:

At resonance: $X_L = X_C \rightarrow V_L = -V_C \rightarrow$ they cancel.

12. A capacitor of $20 \mu\text{F}$ is connected to an AC supply of 220 V, 50 Hz. Capacitive reactance is:

- A. 63.6Ω
- B. 159Ω
- C. 100Ω
- D. 200Ω

Answer: B

Explanation:

$X_C = 1 / (2\pi fC) = 1 / (2 \times \pi \times 50 \times 20 \times 10^{-6}) \approx 159.15 \Omega$ Rechecking:

$X_C = 1 / (2 \times \pi \times 50 \times 20 \times 10^{-6}) = 159.15 \Omega$

13. The instantaneous current in an AC circuit is $i = 3 \sin(100\pi t)$. What is the time period?

- A. 0.02 s
- B. 0.01 s
- C. 0.05 s
- D. 0.1 s

Answer: A

Explanation:

$\omega = 100\pi \rightarrow \omega = 2\pi f \rightarrow f = 50 \text{ Hz} \rightarrow T = 1/f = 0.02 \text{ s}$

14. In an LCR series circuit, at resonance, the current amplitude is maximum because:

- A. Voltage across L is zero
- B. Net reactance is zero
- C. Resistance becomes zero
- D. Capacitance becomes infinite

Answer: B

Explanation:

At resonance: $X_L = X_C \rightarrow$ Net reactance = 0 $\rightarrow Z = R$ (minimum) $\rightarrow I$ is max.

15. An inductor and a resistor are connected in series to an AC supply. The power factor of this circuit lies between:

- A. 0 and 1
- B. 0 and -1
- C. 1 and ∞
- D. -1 and 0

Answer: A

Explanation:

In R-L circuit, current lags voltage \rightarrow Power factor $< 1, > 0$

16. A resistor of $100\ \Omega$, an inductor of 0.5 H , and a capacitor of $100\ \mu\text{F}$ are connected in series with an AC supply of 220 V and 50 Hz . What is the impedance of the circuit?

- A. $100\ \Omega$
- B. $200\ \Omega$
- C. $50\ \Omega$
- D. $0\ \Omega$

Answer: A

Explanation:

At resonance, $X_L = X_C$, so net reactance = 0

Impedance $Z = R = 100\ \Omega$

17. The average power consumed in a pure inductor connected to an AC source is:

- A. Maximum
- B. Zero
- C. Minimum but not zero
- D. Depends on frequency

Answer: B

Explanation:

In a pure inductor, current lags voltage by 90° , so power factor = 0 \rightarrow Power = 0

18. In an AC circuit, voltage leads current by 90° . The circuit contains:

- A. Only resistance
- B. Only inductor
- C. Only capacitor
- D. Resistance and inductor

Answer: C

Explanation:

In a purely capacitive circuit, current leads voltage by $90^\circ \rightarrow$ Voltage lags by 90°

19. If an AC source is connected to a pure resistor, what will be the shape of the current vs time graph?

- A. Sine wave in phase with voltage
- B. Sine wave lagging voltage
- C. Sine wave leading voltage
- D. Square wave

Answer: A

Explanation:

In a resistive circuit, voltage and current are in phase \rightarrow Both are sine waves

20. The frequency of AC voltage used in India is:

- A. 60 Hz
- B. 110 Hz
- C. 50 Hz
- D. 220 Hz

Answer: C

Explanation:

Standard frequency in India = 50 Hz

21. A transformer works on the principle of:

- A. Ohm's law
- B. Mutual induction
- C. Self-induction
- D. Electromagnetic force

Answer: B

Explanation:

Transformers use mutual induction between two coils to transfer energy

22. In an AC circuit with $R = 10\ \Omega$, $L = 0.1\ \text{H}$, and $f = 50\ \text{Hz}$, what is the power factor?

- A. 0.5
- B. 1
- C. 0
- D. 0.302

Answer: D

Explanation:

$$X_L = 2\pi fL = 31.4\ \Omega, Z = \sqrt{R^2 + X_L^2} = \sqrt{100 + 985.96} \approx 32.97$$

$$\cos\phi = R / Z = 10 / 32.97 \approx 0.303 \rightarrow \text{Correction: Not } 0.707$$

Rechecking:

$$X_L = 31.4, R = 10 \rightarrow Z = \sqrt{10^2 + 31.4^2} = \sqrt{100 + 985.96} \approx 33.1$$

$$\cos\phi = 10 / 33.1 \approx 0.302$$

23. A choke coil works on the principle of:

- A. Capacitance
- B. Resistance
- C. Inductance
- D. Conductance

Answer: C

Explanation:

A choke coil uses inductance to block high-frequency AC while allowing DC

24. What is the unit of reactance?

- A. Henry
- B. Ohm
- C. Farad
- D. Volt

Answer: B

Explanation:

Reactance is measured in ohms (Ω), like resistance

25. What will be the current in a $10\ \Omega$ resistor connected to a 220 V, 50 Hz AC supply? (RMS current)

- A. 22 A
- B. 15.6 A
- C. 31.1 A
- D. 220 A

Answer: A

Explanation:

$$I_{\text{rms}} = V_{\text{rms}} / R = 220 / 10 = 22\ \text{A}$$

26. Which of the following changes will increase the capacitive reactance of a circuit?

- A. Increasing capacitance
- B. Increasing frequency
- C. Decreasing frequency
- D. Increasing voltage

Answer: C

Explanation:

$$X_C = 1 / (2\pi fC) \rightarrow X_C \propto 1/f \rightarrow \text{Decreasing } f \text{ increases } X_C$$

27. A circuit draws power only when the phase difference between current and voltage is:

- A. 0°
- B. 90°
- C. 45°
- D. 180°

Answer: A

Explanation:

$P = VI \cos \phi \rightarrow$ For max power, $\cos \phi = 1 \rightarrow \phi = 0^\circ$

28. The average power consumed in a purely resistive AC circuit is given by:

- A. $V \times I$
- B. $(1/2) VI$
- C. $V_{\text{rms}} \times I_{\text{rms}}$
- D. Zero

Answer: C

Explanation:

$P_{\text{avg}} = V_{\text{rms}} \times I_{\text{rms}}$ in resistive circuit

29. What is the role of the core in a transformer?

- A. Increases resistance
- B. Reduces current
- C. Provides path for magnetic flux
- D. Converts AC to DC

Answer: C

Explanation:

The iron core provides a low reluctance path for magnetic flux between coils

30. A transformer has 500 turns in primary and 50 in secondary. If input voltage is 220 V, output voltage is:

- A. 2200 V
- B. 22 V
- C. 110 V
- D. 440 V

Answer: B

Explanation:

$V_s / V_p = N_s / N_p \rightarrow V_s = (50/500) \times 220 = 22 \text{ V}$

31. In a series LCR circuit, resonance occurs when

- A. $X_L = X_C$
- B. $X_L > X_C$
- C. $X_C > X_L$
- D. $R = 0$

Answer: A

Explanation: At resonance, inductive and capacitive reactances are equal in magnitude and cancel each other, i.e., $X_L = X_C$.

32. At resonance, the power factor of an LCR series circuit is

- A. 0
- B. 1
- C. Less than 1
- D. Greater than 1

Answer: B

Explanation: At resonance, voltage and current are in phase. So, the power factor = $\cos(0^\circ) = 1$.

33. In a transformer, the efficiency is defined as

- A. Output voltage / Input voltage
- B. Input power / Output power
- C. Output power / Input power
- D. Input current / Output current

Answer: C

Explanation: Efficiency (η) = Output power / Input power $\times 100\%$.

34. A transformer has 100% efficiency. If the primary coil draws 200 W, what is the power output of the secondary coil?

- A. 100 W
- B. 200 W
- C. 400 W
- D. 0 W

Answer: B

Explanation: If efficiency is 100%, then input power = output power = 200 W.

35. The phase difference between current and voltage in a purely capacitive circuit is

- A. 0 degrees
- B. 90 degrees (current leads)
- C. 90 degrees (current lags)
- D. 180 degrees

Answer: B

Explanation: In a purely capacitive circuit, current leads voltage by 90 degrees.

36. In an AC circuit, the instantaneous current is $i = 5 \sin(100\pi t)$. The frequency is

- A. 50 Hz
- B. 100 Hz
- C. 25 Hz
- D. 200 Hz

Answer: A

Explanation: $\omega = 100\pi = 2\pi f \rightarrow f = \omega / (2\pi) = 100\pi / 2\pi = 50 \text{ Hz}$.

37. In a transformer, if the number of turns in the secondary is double that of the primary, the transformer is

- A. Step-down
- B. Step-up
- C. Ideal
- D. Inverse

Answer: B

Explanation: Secondary turns > primary turns means it's a step-up transformer.

38. In a purely inductive AC circuit, the current

- A. Is in phase with voltage

- B. Leads the voltage by 90 degrees
- C. Lags the voltage by 90 degrees
- D. Leads the voltage by 180 degrees

Answer: C

Explanation: In an inductive circuit, current lags behind voltage by 90 degrees.

39. The function of a capacitor in an AC circuit is to

- A. Increase current
- B. Decrease resistance
- C. Introduce capacitive reactance
- D. Act as fuse

Answer: C

Explanation: A capacitor introduces capacitive reactance $X_C = 1 / (2\pi fC)$.

40. The RMS value of AC current is equal to

- A. Peak current
- B. Half of peak current
- C. $I_0 / \sqrt{2}$
- D. $\sqrt{2} \times I_0$

Answer: C

Explanation: RMS value = $I_0 / \sqrt{2}$, where I_0 is the peak current.

41. A 10 microfarad capacitor is connected to a 50 Hz AC supply. What is the capacitive reactance?

- A. 318 ohms
- B. 106 ohms
- C. 636 ohms
- D. 159 ohms

Answer: A

Explanation: $X_C = 1 / (2 \times \pi \times f \times C) = 1 / (2 \times 3.14 \times 50 \times 10 \times 10^{-6}) \approx 318$ ohms.

42. For an ideal transformer, the ratio of voltages is equal to the ratio of

- A. Currents
- B. Resistances
- C. Turns
- D. Frequencies

Answer: C

Explanation: $V_2 / V_1 = N_2 / N_1$ (voltage ratio = turn ratio).

43. What is the average value of an AC over a complete cycle?

- A. V_0
- B. 0
- C. $V_0 / \sqrt{2}$
- D. $V_0 / 2$

Answer: B

Explanation: The average value of a sine wave over a full cycle is zero.

44. In an LCR circuit, maximum current flows at

- A. High frequency
- B. Low frequency
- C. Resonant frequency
- D. Zero frequency

Answer: C

Explanation: At resonance, impedance is minimum, so current is maximum.

45. The quality factor (Q) of a resonant circuit is a measure of

- A. Energy stored / Energy dissipated per cycle
- B. Voltage / Current
- C. Current / Voltage
- D. Resistance / Inductance

Answer: A

Explanation: $Q = 2\pi \times (\text{energy stored} / \text{energy dissipated per cycle})$.