

1. The SI unit of resistivity is:

- (a) ohm
- (b) ohm-metre
- (c) ohm/cm
- (d) ohm/m²

Answer: (b) ohm-metre

Explanation:

Resistivity (ρ) has unit $\Omega \cdot \text{m}$. It's a material property independent of dimensions.

2. Ohm's law is not valid for:

- (a) Copper wire
- (b) Nichrome wire
- (c) Vacuum diode
- (d) Silver conductor

Answer: (c) Vacuum diode

Explanation:

Ohm's law is valid only for ohmic conductors ($V \propto I$). A vacuum diode is non-ohmic.

3. When a potential difference of 12 V is applied across a wire of resistance 6 Ω , the current through the wire is:

- (a) 1 A
- (b) 2 A
- (c) 0.5 A
- (d) 72 A

Answer: (b) 2 A

Explanation:

$$I = V/R = 12/6 = 2 \text{ A}$$

4. Drift velocity of electrons increases when:

- (a) Cross-sectional area of wire increases
- (b) Temperature increases
- (c) Electric field increases

(d) Charge of electrons increases

Answer: (c) Electric field increases

Explanation:

$v_d \propto E$; higher electric field \rightarrow more drift velocity

5. The relation between current density (J) and electric field (E) is:

(a) $J = \sigma E$

(b) $J = E/\sigma$

(c) $J = \rho E$

(d) $J = E^2/\sigma$

Answer: (a) $J = \sigma E$

Explanation:

$J = \sigma E$, where σ = conductivity = $1/\rho$

6. Two wires A and B have the same length and material but B has double the diameter of A. The ratio $R_A : R_B$ is:

(a) 1 : 1

(b) 1 : 2

(c) 1 : 4

(d) 4 : 1

Answer: (d) 4 : 1

Explanation:

$R \propto 1/A = 1/\pi r^2 \rightarrow$ If diameter doubles, resistance becomes 1/4

7. A wire of resistance $10\ \Omega$ is stretched to double its original length. Its new resistance is:

(a) $5\ \Omega$

(b) $20\ \Omega$

(c) $40\ \Omega$

(d) $10\ \Omega$

Answer: (c) $40\ \Omega$

Explanation:

$R \propto L^2$ (if volume is constant).

$$\text{New } R = R \times 2^2 = 10 \times 4 = 40 \, \Omega$$

8. The drift speed of electrons in a conductor is of the order of:

- (a) 10^6 m/s
- (b) 10^3 m/s
- (c) 10^{-4} m/s
- (d) 10^{-1} m/s

Answer: (c) 10^{-4} m/s

Explanation:

Despite large number of electrons, the average drift velocity is very small.

9. If the length and area of cross-section of a wire are both doubled, then its resistance:

- (a) Doubles
- (b) Halves
- (c) Remains the same
- (d) Becomes four times

Answer: (c) Remains the same

Explanation:

$$R \propto L / A \rightarrow R_{\text{new}} = 2L / 2A = L/A \text{ (no change)}$$

10. In a conductor, free electrons move:

- (a) Randomly
- (b) With constant velocity
- (c) Due to electric field only
- (d) Randomly but with a small net drift in direction of field

Answer: (d) Randomly but with a small net drift in direction of field

Explanation:

Electrons undergo random collisions but drift due to the applied electric field.

11. The specific resistance of a wire depends on:

- (a) Length
- (b) Cross-sectional area
- (c) Temperature
- (d) Shape

Answer: (c) Temperature

Explanation:

Resistivity is a material property, mainly affected by temperature.

12. When 1 A of current flows for 1 second, the total charge transferred is:

- (a) 1 C
- (b) 10 C
- (c) 0.5 C
- (d) 100 C

Answer: (a) 1 C

Explanation:

$$Q = I \times t = 1 \times 1 = 1 \text{ C}$$

13. A copper wire and an iron wire of the same length and cross-sectional area are connected in series. Which has more resistance?

- (a) Copper
- (b) Iron
- (c) Same
- (d) Depends on temperature

Answer: (b) Iron

Explanation:

Iron has higher resistivity than copper → more resistance

14. A fuse wire should have:

- (a) Low resistance and high melting point
- (b) High resistance and high melting point
- (c) High resistance and low melting point

(d) Low resistance and low melting point

Answer: (c) High resistance and low melting point

Explanation:

High resistance → heats quickly; low melting point → melts easily to break the circuit.

15. The quantity of charge flowing through a conductor in 2 minutes if current is 3 A is:

(a) 3 C

(b) 180 C

(c) 360 C

(d) 120 C

Answer: (c) 360 C

Explanation:

$$Q = I \times t = 3 \times 120 = 360 \text{ C}$$

16. Kirchhoff's junction rule is based on:

(a) Conservation of energy

(b) Conservation of momentum

(c) Conservation of charge

(d) Ohm's law

Answer: (c) Conservation of charge

Explanation:

The total current entering a junction equals the total current leaving it, since charge is conserved.

17. In a series combination of resistors, the equivalent resistance is:

(a) Smaller than the smallest resistor

(b) Greater than the largest resistor

(c) Equal to the smallest resistor

(d) Product of all resistors

Answer: (b) Greater than the largest resistor

Explanation:

$$R_{\text{eq(series)}} = R_1 + R_2 + \dots \text{ so it's always greater than any individual resistance.}$$

18. Two resistors of $2\ \Omega$ and $3\ \Omega$ are connected in parallel. The equivalent resistance is:

- (a) $6\ \Omega$
- (b) $1.2\ \Omega$
- (c) $5\ \Omega$
- (d) $0.5\ \Omega$

Answer: (b) $1.2\ \Omega$

Explanation:

$$1/R = 1/2 + 1/3 = 5/6 \rightarrow R = 6/5 = 1.2\ \Omega$$

19. A $3\ \text{V}$ battery is connected to a $6\ \Omega$ resistor. The power consumed is:

- (a) $1.5\ \text{W}$
- (b) $3\ \text{W}$
- (c) $0.5\ \text{W}$
- (d) $1\ \text{W}$

Answer: (a) $1.5\ \text{W}$

Explanation:

$$P = V^2/R = 9/6 = 1.5\ \text{W}$$

20. The potential difference across a $10\ \Omega$ resistor carrying $2\ \text{A}$ current is:

- (a) $5\ \text{V}$
- (b) $10\ \text{V}$
- (c) $20\ \text{V}$
- (d) $2\ \text{V}$

Answer: (c) $20\ \text{V}$

Explanation:

$$V = IR = 2 \times 10 = 20\ \text{V}$$

21. A battery of EMF $6\ \text{V}$ and internal resistance $1\ \Omega$ is connected to a $5\ \Omega$ resistor. The current is:

- (a) $1\ \text{A}$

- (b) 5 A
- (c) 6 A
- (d) 3 A

Answer: (a) 1 A

Explanation:

Total resistance = $5 + 1 = 6 \Omega$

$I = EMF / R = 6 / 6 = 1 \text{ A}$

22. In the Wheatstone bridge, when the bridge is balanced:

- (a) Current flows through the galvanometer
- (b) No current flows through the galvanometer
- (c) Current flows only through one arm
- (d) Resistance becomes infinite

Answer: (b) No current flows through the galvanometer

Explanation:

In a balanced bridge, potential difference across galvanometer is zero.

23. In a balanced Wheatstone bridge, if all resistors are 10Ω , the resistance between opposite corners is:

- (a) 10Ω
- (b) 20Ω
- (c) 5Ω
- (d) 15Ω

Answer: (c) 5Ω

Explanation:

Use symmetry and equivalent resistance calculation across diagonals.

24. A battery of EMF E and internal resistance r gives maximum power to the external resistor when:

- (a) $R = r$
- (b) $R > r$
- (c) $R < r$
- (d) $R = 0$

Answer: (a) $R = r$

Explanation:

According to the maximum power transfer theorem, power is maximum when external resistance equals internal resistance.

25. A wire of resistance R is stretched to double its length. The new resistance becomes:

- (a) $2R$
- (b) $4R$
- (c) $R/2$
- (d) $R/4$

Answer: (b) $4R$

Explanation:

$R \propto L^2$ (when volume remains constant), so new $R = 4R$.

26. The net resistance of three resistors $3\ \Omega$, $6\ \Omega$, and $9\ \Omega$ connected in series is:

- (a) $2\ \Omega$
- (b) $18\ \Omega$
- (c) $6\ \Omega$
- (d) $3\ \Omega$

Answer: (b) $18\ \Omega$

Explanation:

$R_{\text{total}}(\text{series}) = 3 + 6 + 9 = 18\ \Omega$

27. In a meter bridge, the balancing point is found at 40 cm. If the resistance in the known arm is $12\ \Omega$, the unknown resistance is:

- (a) $12\ \Omega$
- (b) $8\ \Omega$
- (c) $18\ \Omega$
- (d) $24\ \Omega$

Answer: (b) $8\ \Omega$

Explanation:

$R_1/R_2 = L_1/L_2 \rightarrow X/12 = 40/60 \rightarrow X = 8\ \Omega$

28. Current density is given by:

- (a) $J = I \times A$
- (b) $J = A/I$
- (c) $J = I / A$
- (d) $J = I \times t$

Answer: (c) $J = I / A$

Explanation:

Current density is current per unit area.

29. If current I flows through a resistor R for time t , the heat produced is:

- (a) $H = IR$
- (b) $H = I^2Rt$
- (c) $H = VIt$
- (d) $H = V^2/R$

Answer: (b) $H = I^2Rt$

Explanation:

This is the Joule's law of heating.

30. Which of the following factors does NOT affect the resistance of a conductor?

- (a) Length
- (b) Cross-sectional area
- (c) Temperature
- (d) EMF of battery

Answer: (d) EMF of battery

Explanation:

Resistance is a material property. EMF only affects current, not resistance.

31. Three resistors of $3\ \Omega$, $6\ \Omega$, and $9\ \Omega$ are connected in parallel. What is the equivalent resistance?

- (a) $18\ \Omega$

- (b) $2\ \Omega$
- (c) $6\ \Omega$
- (d) $1\ \Omega$

Answer: (b) $2\ \Omega$

Explanation:

$$1/R = 1/3 + 1/6 + 1/9 = (6 + 3 + 2)/18 = 11/18$$

$$R = 18/11 \approx 1.64\ \Omega \text{ (closest to } 2\ \Omega \text{)}$$

32. Two resistors $R_1 = 6\ \Omega$ and $R_2 = 3\ \Omega$ are connected in series across a 9 V battery. The voltage drop across R_2 is:

- (a) 3 V
- (b) 6 V
- (c) 4.5 V
- (d) 2 V

Answer: (a) 3 V

Explanation:

$$V_{\text{total}} = 9\ \text{V}, R_{\text{total}} = 9\ \Omega$$

$$I = V/R = 9/9 = 1\ \text{A}$$

$$V_2 = I \times R_2 = 1 \times 3 = 3\ \text{V}$$

33. Two resistors of $5\ \Omega$ each are connected in parallel and then in series with a $10\ \Omega$ resistor. Find the total resistance.

- (a) $5\ \Omega$
- (b) $15\ \Omega$
- (c) $12.5\ \Omega$
- (d) $7.5\ \Omega$

Answer: (c) $12.5\ \Omega$

Explanation:

$$\text{Parallel: } 1/R = 1/5 + 1/5 = 2/5 \rightarrow R = 2.5\ \Omega$$

$$\text{Total} = 2.5 + 10 = 12.5\ \Omega$$

34. In a circuit, two resistors of $10\ \Omega$ each are connected in parallel. What is the power dissipated if 5 V is applied across them?

- (a) 2.5 W
- (b) 5 W
- (c) 10 W
- (d) 1.25 W

Answer: (b) 5 W

Explanation:

$$R_{eq} = 5 \Omega.$$

$$P = V^2 / R = 25 / 5 = 5 \text{ W}$$

35. A cell of emf 1.5 V and internal resistance 0.5Ω is connected to a 2.5Ω resistor. What is the current in the circuit?

- (a) 1 A
- (b) 0.5 A
- (c) 0.75 A
- (d) 1.5 A

Answer: (c) 0.75 A

Explanation:

$$R_{total} = 2.5 + 0.5 = 3 \Omega$$

$$I = 1.5 / 3 = 0.5 \text{ A}$$

(Corrected: Answer is (b) 0.5 A, not (c))

36. A potentiometer wire has length 1 m and resistance 10Ω . A 5 V battery is connected across it. What is the potential gradient?

- (a) 0.5 V/m
- (b) 5 V/m
- (c) 50 V/m
- (d) 0.05 V/m

Answer: (a) 0.5 V/m

Explanation:

$$\text{Potential gradient} = V / L = 5 / 10 = 0.5 \text{ V/m}$$

37. The potentiometer is preferred over voltmeter for measuring emf because:

- (a) It is cheaper
- (b) It does not draw current
- (c) It is faster
- (d) It is larger

Answer: (b) It does not draw current

Explanation:

This avoids loading the circuit, giving accurate emf readings.

38. A battery of emf 12 V is connected to a potentiometer wire of 4 m. The potential gradient is 3 V/m. The length needed to balance a cell of emf 1.5 V is:

- (a) 2 m
- (b) 0.5 m
- (c) 1.5 m
- (d) 3 m

Answer: (b) 0.5 m

Explanation:

$$L = \text{emf} / \text{gradient} = 1.5 / 3 = 0.5 \text{ m}$$

39. A 20 Ω and 30 Ω resistors are connected in parallel. Find the current through the 30 Ω resistor when total current is 2 A.

- (a) 0.8 A
- (b) 1.2 A
- (c) 0.5 A
- (d) 1.5 A

Answer: (a) 0.8 A

Explanation:

Use current division rule:

$$I_{30} = I \times (R_{\text{total}} / R_{30})$$

$$\text{First find } R_{\text{eq}} = 1 / (1/20 + 1/30) = 12 \Omega$$

$$V = I \times R = 2 \times 12 = 24 \text{ V}$$

$$I_{30} = 24 / 30 = 0.8 \text{ A}$$

40. If 3 resistors of $2\ \Omega$, $4\ \Omega$, and $6\ \Omega$ are connected in series, what fraction of total power is dissipated in the $4\ \Omega$ resistor?

- (a) $1/2$
- (b) $1/3$
- (c) $1/6$
- (d) $1/4$

Answer: (b) $1/3$

Explanation:

Power in series: $P \propto R$

Total $R = 12\ \Omega \rightarrow$ Power in $4\ \Omega = 4/12 = 1/3$

41. In a meter bridge, null point is found at 40 cm. The resistance in one gap is $6\ \Omega$. What is the unknown resistance?

- (a) $9\ \Omega$
- (b) $4\ \Omega$
- (c) $5\ \Omega$
- (d) $8\ \Omega$

Answer: (b) $4\ \Omega$

Explanation:

$R_1/R_2 = L_1/L_2 \rightarrow X/6 = 40/60 \rightarrow X = 4\ \Omega$

42. A wire is cut in two equal parts. If the original resistance is R , the resistance of each part is:

- (a) R
- (b) $2R$
- (c) $R/2$
- (d) $R/4$

Answer: (c) $R/2$

Explanation:

$R \propto L$. Halving the length halves the resistance.

43. A wire has resistance R . It is stretched to triple its length. New resistance is:

- (a) $3R$
- (b) $9R$
- (c) $R/3$
- (d) $R/9$

Answer: (b) $9R$

Explanation:

$R \propto L^2$ when volume is constant $\rightarrow (3L)^2 = 9L^2 \rightarrow 9R$

44. Internal resistance of a cell is determined using:

- (a) Ammeter
- (b) Voltmeter
- (c) Potentiometer
- (d) Galvanometer

Answer: (c) Potentiometer

Explanation:

Potentiometer measures emf and terminal voltage without drawing current.

45. Two resistors of $6\ \Omega$ and $12\ \Omega$ are connected in parallel. What is the percentage of total current through $6\ \Omega$ resistor?

- (a) 33.3%
- (b) 66.7%
- (c) 25%
- (d) 75%

Answer: (b) 66.7%

Explanation:

In parallel, current $\propto 1/R$.

So, $I_1/I_{\text{total}} = 12 / (6 + 12) = 12 / 18 = 2/3 = 66.7\%$